

This ULU

The *ULU.06 Dual JK flip-flop* provides two JK flip-flops. These can be used in several ways, as described further in this datasheet.

Used parts

Only standard parts are used:

1x casing 80 x 50 x 20mm;	2x resistor to dim the LEDs;
10x 1-bit signal connector;	2x LED holder;
10x black O-ring 9 x 5 x 2mm;	2x micro (G6K-2F-Y-5VDC) relay;
1x power socket;	2x fly back diode (1N4148);
1x Arduino Nano;	2x 1-pole ON-OFF-ON switch;
6x 10K pull-down resistor;	1x 11 x 8-hole experiment PCB
2x 3mm LED;	

Construction

The standard ULU specifications are applicable and given in the datasheet *ULU.00 – Common specifications*.

 


Figure 1 – Drill guide

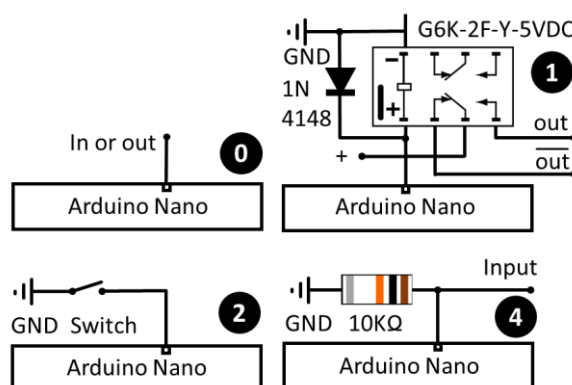


Figure 2 – Arduino interfaces


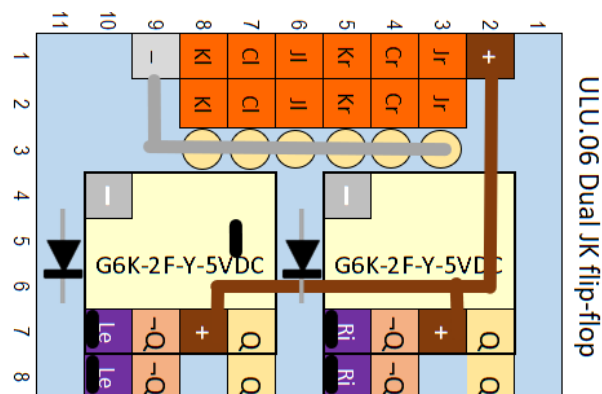


Figure 3 – Layout relay & resistor PCB

 

Figure 4 – Finished ULU



Port	Con.	Rest.	Func.	Interface	Signal
1. D2	●		I	4	Jright
2. D3	●		I	4	Kright
3. D4	●		I	4	Kright
4. D5	⏏		T	2	Kright = \overline{Jright}
5. D6	□		O	1	Qright
6. D7	●		I	4	Jleft
7. D8	●		I	4	Kleft
8. D9	●		I	4	Kleft
9. D10	⏏		T	2	Kleft = \overline{Jleft}
10. D11	□		O	1	Qleft
11. D13		O	L		Hartbeat LED
12. A0	⏏		I	2	OneSocketleft
13. A1	⏏		I	2	OneSocketright
14. +5V	⊙	I	I	0	DC +5V
15. GND	⊙	I	I	0	GND

Input, Output, Led, SPI, Toggle switch, Rotary switch

Figure 5 – Pinout Arduino Nano

Trigger	Inputs		Output						Inference		
			Present State		Intermediate		Next State				
CLK	J	K	Q	\bar{Q}	M ₁	M ₂	Q	\bar{Q}			
↑	0	0	0	1	0	1	Latched		No Change		
↓			0	1	Latched		0	1			
↑			1	0	Latched		1	0			
↓			1	0	Latched		1	0			
↑	0	1	0	1	0	1	Latched		Reset		
↓			0	1	Latched		0	1			
↑			1	0	0	1	Latched			0	1
↓			1	0	Latched		0	1			
↑	1	0	0	1	1	0	Latched		Set		
↓			0	1	Latched		1	0			
↑			1	0	1	0	Latched			1	0
↓			1	0	Latched		1	0			
↑	1	1	0	1	1	0	Latched		Toggles		
↓			0	1	Latched		1	0			
↑			1	0	0	1	Latched				
↓			1	0	Latched		0	1			

Figure 6 – Truth table JK flip-flop

 


Figure 7 – Various states of PCB fabrication

First the PCB is cut to size, then all the resistors, diodes and wires are soldered. Input wires are soldered on the top side, output (relay) wires on the bottom side. After that, the wires for the Arduino are cut to

length and soldered to the Arduino board. The Arduino Nano pinout is given in Figure 5. After that, the relays can be easily soldered on the top PCB side and will connect to the wires on the bottom side.

Make sure the top of PCB and the top of the Arduino board can be folded towards each other. A piece of tape on the Arduino bottom side will prevent unwanted electrical contacts. This is shown in Figure 7

Both LEDs have their (long) + pin left intact and soldered them to the (yellow) output connector. The resistor is soldered to the (short) – pin. The common of both switches are connected to the ground (-) and the contact that makes the switch on when the rocker is set downwards, is connected to the Arduino.

If there is a risk that the PCB makes unwanted contact with the connectors, put some heat shrink tube on those connectors.

Usage

The JK flip-flop has three inputs and one output Q. The other output \bar{Q} is the inverse of Q (NOT Q). The basic layout of the JK flip flop is drawn in Figure 8. This ULU can be used in three ways:

1. Set/reset flip-flop

Set: when J and clock are set to 1 simultaneously, the output Q will become 1 and \bar{Q} will become 0.

Reset/clear: when K and clock are set to 1 simultaneously, the output Q will become 0 and \bar{Q} 1.

This type of flip-flop can be used to ‘remember’ the input. See Figure 9.

2. Toggle flip-flop

When J, K and clock are set to 1 simultaneously, the output Q will toggle. If it was 0, it will become 1 and if it was 1 it will become 0.

This type of flip-flop can be used to make a counter. See Figure 10.

3. Memory/data storage

When K is set to the inverse of J (Not J) the flip-flop can used to store data. When the data line is attached to the K and the clock is set to 1, the flip-flop will remember the offered data value. To facilitate this type of flip-flop, a switch is provided. When the switch is set to the top, the K input is kept equal to the inverse of J.

This type of flip-flop can be used as a one-bit register or a shift register. See Figure 11.

 


Figure 8 – The JK flip-flop Figure 9 – Using the JK flip-flop

 
 


Figure 10 – Counter

 
 


Figure 11 – Shift register

For easy use of this ULU there is a single socket modus. For that, the switch need to be in the center position. This modus works exactly as the JK flip-flop modus, apart from the fact that only one line is used for controlling the flip-flop. The way to control the flip-flop in this modus is shown in Figure 12.

 


Figure 12 – Single socket control


 


Figure 13 – Connectors & controls

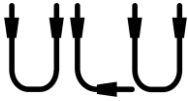

Arduino Nano solder check

```
/* ULU.06 Dual JK flip-flop - solder check */
/* CC BY-NC-SA Jeroen Brinkman */

bool triggerleft, triggerright; // booleans
jleft, lastjleft, cleft, lastcleft, kleft, lastkleft, setleft, qleft, switchleft; // left variables
jright, lastjright, cright, lastcright, kright, lastkright, setright, qright, switchright; // right variables

#define BOUNCE 8
#define WAIT 150
#define RJ 2
#define RC 3
#define RK 4
#define RU 5
#define RQ 6
#define LJ 7
#define LC 8
#define LK 9
#define LU 10
#define LQ 11
#define LD A0
#define RD A1
#define HEART 13

void setup() {
  /* Define I/O pins */
  pinMode(RJ, INPUT);
  pinMode(RC, INPUT);
  pinMode(RK, INPUT);
  pinMode(RU, INPUT_PULLUP);
  pinMode(RQ, OUTPUT);
  pinMode(LJ, INPUT);
  pinMode(LC, INPUT);
  pinMode(LK, INPUT);
  pinMode(LD, INPUT_PULLUP);
  pinMode(LQ, OUTPUT);
  pinMode(HEART, OUTPUT); // blinking led showing the program heartbeat
  pinMode(RD, INPUT);
  pinMode(LD, INPUT);

  /* Every ULU with an Arduino introduces itself. This one uses blinking leds */
  digitalWrite(LQ, HIGH); delay(WAIT);
  digitalWrite(LQ, LOW); digitalWrite(RQ, HIGH); delay(WAIT);
  digitalWrite(LQ, HIGH); digitalWrite(RQ, LOW); delay(WAIT);
  digitalWrite(LQ, LOW); digitalWrite(RQ, HIGH); delay(WAIT);
  digitalWrite(LQ, HIGH); digitalWrite(RQ, LOW); delay(WAIT);
  digitalWrite(LQ, LOW); digitalWrite(RQ, HIGH); delay(WAIT); digitalWrite(RQ, LOW);
}

void blink(int side, show){
  for (int counter=1; counter <= show; counter = counter+1){
    digitalWrite(side, HIGH);
    delay(150);
    digitalWrite(side, LOW);
    delay(150);
  }
  delay(1000);
}

void loop(){
  digitalWrite(HEART, (millis() / 1000) % 2); //1s heartbeat for the onboard led


  if (!digitalRead(RU) == 1) blink(RQ, 1);
  if (!digitalRead(RD) == 1) blink(RQ, 2);
  if (digitalRead(RJ) == 1) blink(RQ, 3);
  if (digitalRead(RC) == 1) blink(RQ, 4);
  if (digitalRead(RK) == 1) blink(RQ, 5);
  if (!digitalRead(LU) == 1) blink(LQ, 1);
  if (!digitalRead(LD) == 1) blink(LQ, 2);
  if (digitalRead(LJ) == 1) blink(LQ, 3);
  if (digitalRead(LC) == 1) blink(LQ, 4);
  if (digitalRead(LK) == 1) blink(LQ, 5);
}
```

Arduino Nano program

```
/* ULU.06 Dual JK flip-flop - program code */
/* CC BY-NC-SA Jeroen Brinkman */

bool triggerleft, triggerright; // booleans
int i;
int jleft, lastjleft, cleft, lastcleft, kleft, lastkleft, setleft, qleft, switchleft; // left variables
int jright, lastjright, cright, lastcright, kright, lastkright, setright, qright, switchright; // right variables
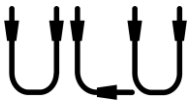
#define BOUNCE 8
#define WAIT 150
#define RJ 2
#define RC 3
#define RK 4
#define RU 5
#define RQ 6
#define LJ 7
#define LC 8
#define LK 9
#define LU 10
#define LQ 11
```



```
#define LD A0
#define RD A1
#define HEART 13

void setup() {
  /* Define I/O pins */
  pinMode(RJ, INPUT);
  pinMode(RC, INPUT);
  pinMode(RK, INPUT);
  pinMode(RU, INPUT_PULLUP);
  pinMode(RQ, OUTPUT);
  pinMode(LJ, INPUT);
  pinMode(LC, INPUT);
  pinMode(LK, INPUT);
  pinMode(LD, INPUT_PULLUP);
  pinMode(LQ, OUTPUT);
  pinMode(HEART, OUTPUT); // blinking led showing the program heartbeat
  pinMode(RD, INPUT);
  pinMode(LD, INPUT);

  /* Every ULU with an Arduino introduces itself. This one uses blinking leds */
  digitalWrite(LQ, HIGH); delay(WAIT);
  digitalWrite(LQ, LOW); digitalWrite(RQ, HIGH); delay(WAIT);
  digitalWrite(LQ, HIGH); digitalWrite(RQ, LOW); delay(WAIT);
  digitalWrite(LQ, LOW); digitalWrite(RQ, HIGH); delay(WAIT);
  digitalWrite(LQ, HIGH); digitalWrite(RQ, LOW); delay(WAIT);
  digitalWrite(LQ, LOW); digitalWrite(RQ, HIGH); delay(WAIT); digitalWrite(RQ, LOW);

  /* Initialize variables */
  triggerleft = false; setleft = 0; qleft = 0;
  lastcleft = 0; lastjleft = 0; lastkleft = 0;
  triggerright = false; setright = 0; qright = 0;
  lastcright = 0; lastjright = 0; lastkright = 0;
}

void loop(){
  digitalWrite(HEART, (millis() / 1000) % 2); //1s heartbeat for the onboard led

  /* read the switches */
  switchright = !digitalRead(RU) + (!digitalRead(RD) * 2);
  switchleft = !digitalRead(LU) + (!digitalRead(LD) * 2);


  /* read the input */
  jleft = 0; kleft = 0; cleft = 0;
  jright = 0; kright = 0; cright = 0;
  for (i = 0; i < BOUNCE; i++) { //debounce routine
    jright += digitalRead(RJ);
    cright += digitalRead(RC);
    kright += digitalRead(RK);
    jleft += digitalRead(LJ);
    cleft += digitalRead(LC);
    kleft += digitalRead(LK);
    delay(1);
  }
  jright = (jright > i / 2) ? 1 : 0;
  cright = (cright > i / 2) ? 1 : 0;
  kright = (kright > i / 2) ? 1 : 0;
  jleft = (jleft > i / 2) ? 1 : 0;
  cleft = (cleft > i / 2) ? 1 : 0;
  kleft = (kleft > i / 2) ? 1 : 0;

  /* Determine right trigger */
  triggerright = ((cright == 0) && (lastcright == 1)) ? true : false;
  if ((switchright == 0) && (lastjright == 1) && (jright == 0)) triggerright = true;
  if ((switchright == 0) && (lastkright == 1) && (kright == 0)) triggerright = true;
  lastjright = jright; lastcright = cright; lastkright = kright;

  /* Determine right action */
  if (switchright == 0) {
    setright = 0;
    if (jright == 1) setright = 1;
    if (cright == 1) setright = 2;
    if (kright == 1) setright = 3;
  } else {
    if (cright == 1) setright = (jright * 2) + kright;
  }

  /* determine & write right output */
  if (triggerright){
    triggerright = false;
    switch (setright) {
      case 0: // NOP
        break;
      case 1: // reset
        qright = 0;
        break;
      case 2: // set
        qright = 1;
        break;
      case 3: // toggle
        qright = (qright == 0) ? 1 : 0;
        break;
    }
  }
  digitalWrite(RQ, (qright == 1) ? HIGH : LOW);
}

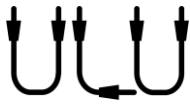/* Determine left trigger */
triggerleft = ((cleft == 0) && (lastcleft == 1)) ? true : false;
if ((switchleft == 0) && (lastjleft == 1) && (jleft == 0)) triggerleft = true;
if ((switchleft == 0) && (lastkleft == 1) && (kleft == 0)) triggerleft = true;
```



```
lastjleft = jleft; lastcleft = cleft; lastkleft = kleft;

/* determine left action */
if (switchleft == 0) {
    setleft = 0;
    if (jleft == 1) setleft = 1;
    if (cleft == 1) setleft = 2;
    if (kleft == 1) setleft = 3;
} else {
    if (cleft == 1) setleft = (jleft * 2) + kleft;
}

/* determine & write left output */
if (triggerleft){
    triggerleft = false;
    switch (setleft) {
        case 0: // NOP
            break;
        case 1: // reset
            qleft = 0;
            break;
        case 2: // set
            qleft = 1;
            break;
        case 3: // toggle
            qleft = (qleft == 0) ? 1 : 0;
            break;
    }
    digitalWrite(RQ, (qleft == 1) ? HIGH : LOW);
}
```